
ASSIGNMENT-1

Name: RITHIKA R

College: Sona College Of Technology

Create a circuit with Piezoalarm, PIR sensor, and temp sensor with the below functionalities:

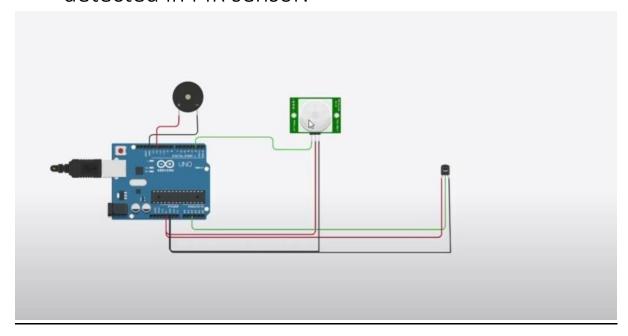- 1. Alarmshouldsoundinonemanneriftempisabove 60 degree Celsius.
- **2.** Alarmshouldsoundwithanotherfrequencyifmotionis detected in PIR sensor.



CODING:


```
void setup()
{
   Serial.begin(9600);
   pinMode(2,INPUT);
```


```
pinMode(12,OUTPUT);
}
void loop()
{
  int motion=digitalRead(2);
  if(motion==1){Serial.println("Moton
  detected");
tone(12,10);
delay(1000);
noTone(12);
delay(1000);
  }
  else{
   Serial.println("Nomotion");
  doubledata=analogRead(A2);
  doublen=data/1024;
  double volt=n*5;
  doubleoff=volt-0.5;
  double temperature=off*100;
  Serial.print("Temperaturedata:");
  Serial.println(temperature);
  if(temperature>60.00)
  {
   tone(12,100);d
```

```
elay(500);noT
one(12);delay(
500);
}
```

}

OUTPUT:

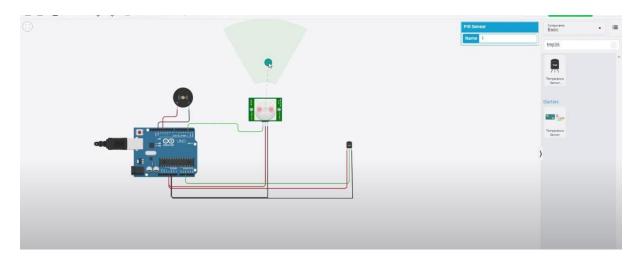

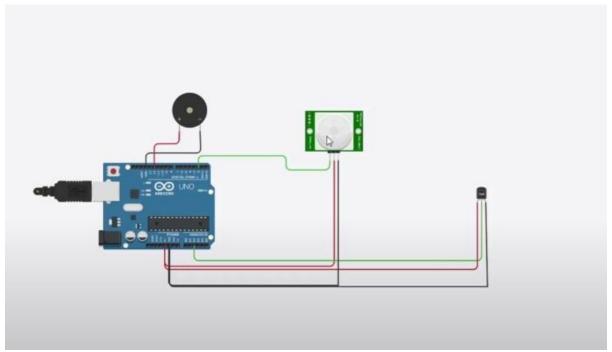

SIMULATIONLINK:

https://drive.google.com/file/d/1WsO0qm42ZsLrhDD1oAiO9JtdkCLeq38Q/view?usp=drivesdk